

7 Segment Display Driver


Design Top Level:

- Inputs
 - `dataIn[15:0]` will be mapped to the switches on the board.
 - `clk` will be connected to the clock pin.
 - `rst` will be connected to a button on the board.
- Outputs
 - `anode[3:0]` will be connected to 7 segment anode pins.
 - `sevenSeg[7:0]` will be connected to each of the seven segment displays.

Design Behavior:

- There are 4 displays. Each 4 bits input out of 16 is assigned for one of the display.
- You need to update the active display within an order. To do that you need 16 bits counter at least. Such that;
- When `counter[15:14] == 00`, you should drive first display and deactivate the rest. To do that you should assign `anode = 4'b0111`;
- When `counter[15:14] == 01`, you should assign `anode = 4'b1011`; to drive second display and deactivate the rest.
- When `counter[15:14] == 10`, you should assign `anode = 4'b1101`; for third one.
- When `counter[15:14] == 11`, you should assign `anode = 4'b1110`; for last one.

Design Behavior:

 

As it can be seen from the picture above, 4 different 4-bit data (max value = F (15)) will be entered from switches and the output should be observed on 7-segment display instantaneously.